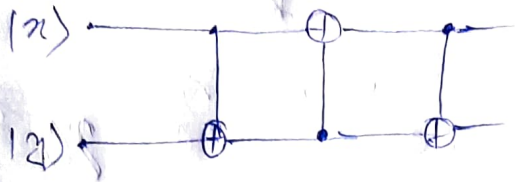


# Assignment ①

Is it possible to

Question ① Implement Swap Gate using single qubit gates only.

Answer



Hence the matrix of this swap gate

looks like = 
$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} = M$$

If possible let  $\begin{bmatrix} \cdot & \cdot \\ \cdot & \cdot \end{bmatrix}$  1-input - 1-output qubit gates  $A \otimes B$  ~~such that~~ with matrices ~~such~~

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \otimes \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \text{ resp.}$$

So  $A \otimes B = M.$

$\Rightarrow \begin{bmatrix} a_{11}B & a_{12}B \\ a_{21}B & a_{22}B \end{bmatrix} = M.$

$\Rightarrow a_{11}b_{12} = 0 \Rightarrow a_{11} = 0 \text{ or } b_{12} = 0$  [ $\because \mathbb{C}$  is a field]

If  $a_{11} = 0 \Rightarrow a_{11}b_{11} = 0$  [ $\because \mathbb{C}$  is a field] — But  $a_{11}b_{11} = 1$

If  $b_{12} = 0 \Rightarrow a_{21}b_{12} = 0$  [ $\because \mathbb{C}$  is a field] — But  $a_{21}b_{12} = 1$

— Contradiction.

So it's not possible to implement swap gate via single input qubit gates.

## AND- Gate Using Toffoli-Gate:-

Truth table.

$x$	$y$	$z$	$z_1$	$z_2$	$z_1 \oplus z_2$
0	0	0	0	0	0
0	1	0	0	1	0
1	0	0	1	0	0
1	1	0	1	1	1
0	0	1	0	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

So, if we put  $z=0$  then we can get easily the AND Gate.

So, the Basic concept of  $x \oplus 0 = x$

Hence, AND Gate  $\oplus 0 =$  AND Gate  
If we  $\oplus 1$  in stead of 0 then it will be NAND Gate.

In a

Very Similar manner we can also

implement other gates.

X-Gate  $\oplus$  0 = X-Gate.

X-Gate  $\oplus$  1 = NOT-X-Gate,